

# ECE 3043 Summer 2018

## Homework Problem Set No 3 for Experiment No. 3

**Due Second Meeting Week of June 4**

1. The excitation for both circuits shown below is  $v_i(t) = 10 \text{ V}u(t)$ . Plot the voltage  $v_o(t)$ , the reactive voltage and current for the two circuits using Mathcad. Plot the circuit variables as  $t$  varies from 0 to two time constants for the circuits.. The values of the circuit components are  $R_1 = 12 \text{ k}\Omega$ ,  $R_2 = 15 \text{ k}\Omega$ ,  $R_3 = 4.3 \text{ k}\Omega$ ,  $L = 3 \text{ mH}$ , and  $C = 0.022 \text{ }\mu\text{F}$ .
2. Make the same plot as in Problem 2 using Matlab.
3. Make the same plot as in Problem 2 using National Instruments SPICE (Multisim).
4. Make the same plot as in Problem 2 using LTSpice (text editor input mode).

